
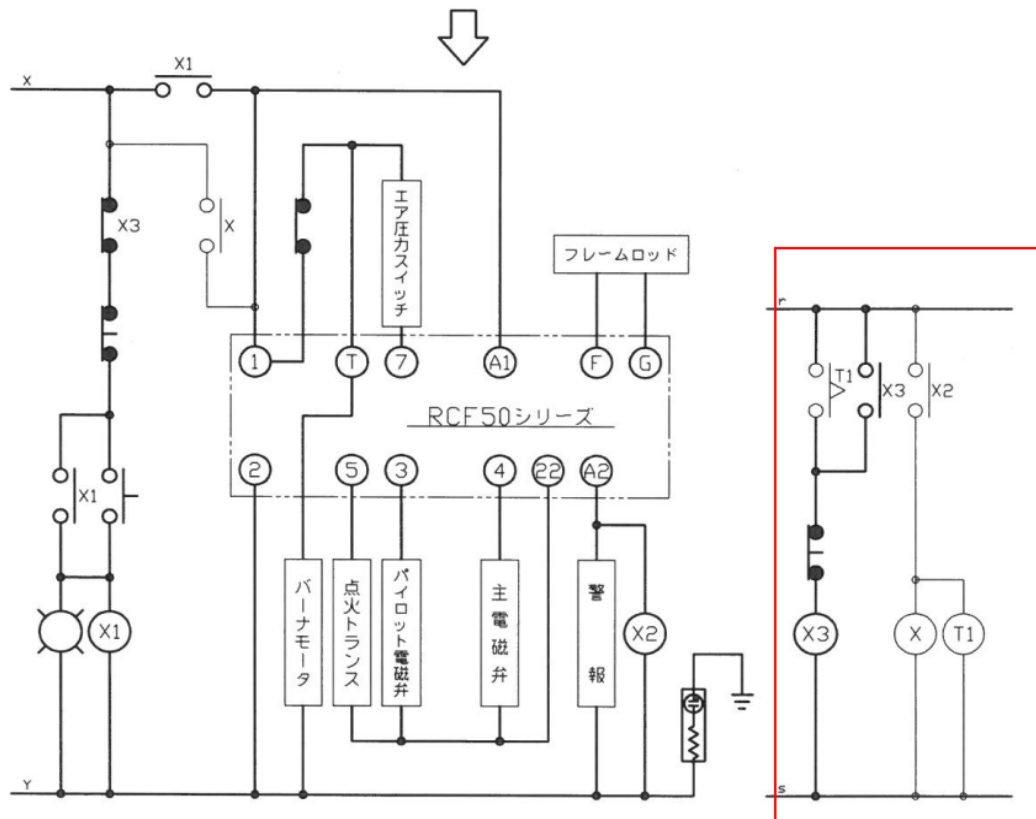


R4750B to RCF502 (or RCF501)


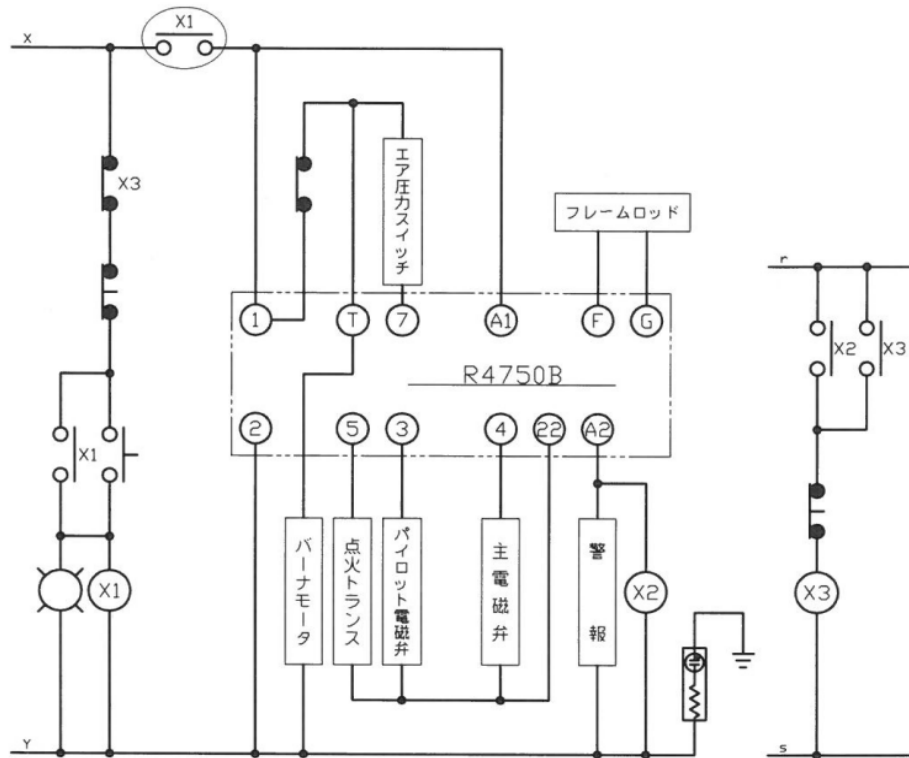
Case 1: Control circuit that Power to Burner control (Terminal 1) is Off when Alarm signal is generated.



Mesure : Add "Delay timer" as T1 and Relay as X. Power to Terminal 1 ON when Alarm is generated.

R4750B to RCF502 (or RCF501)

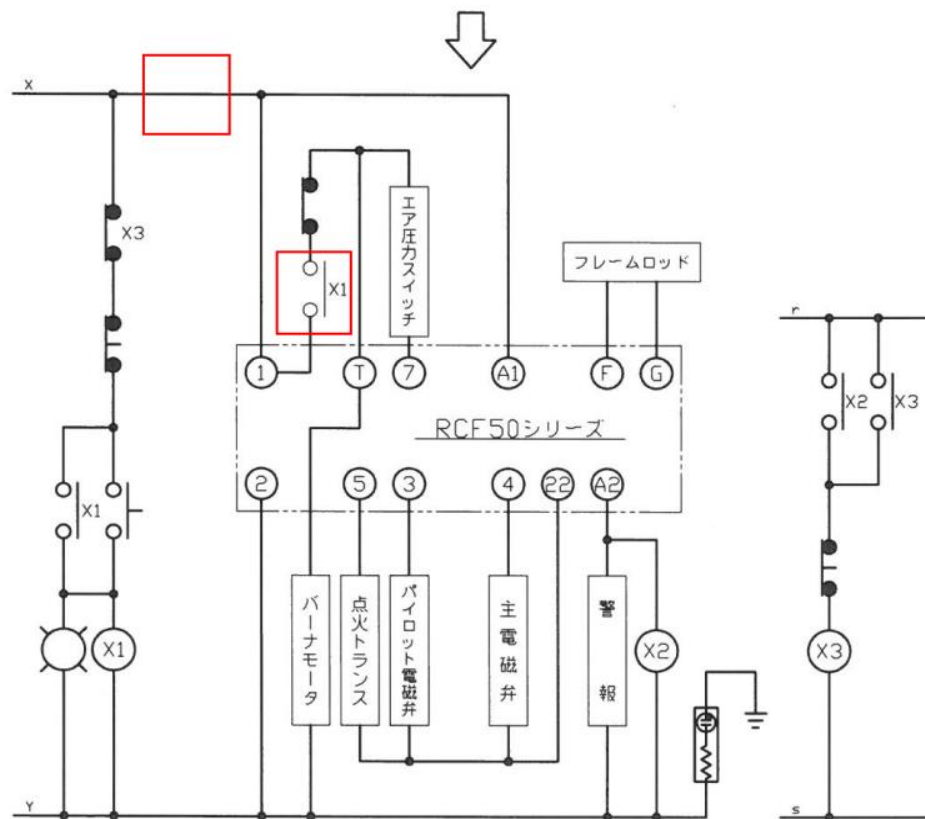
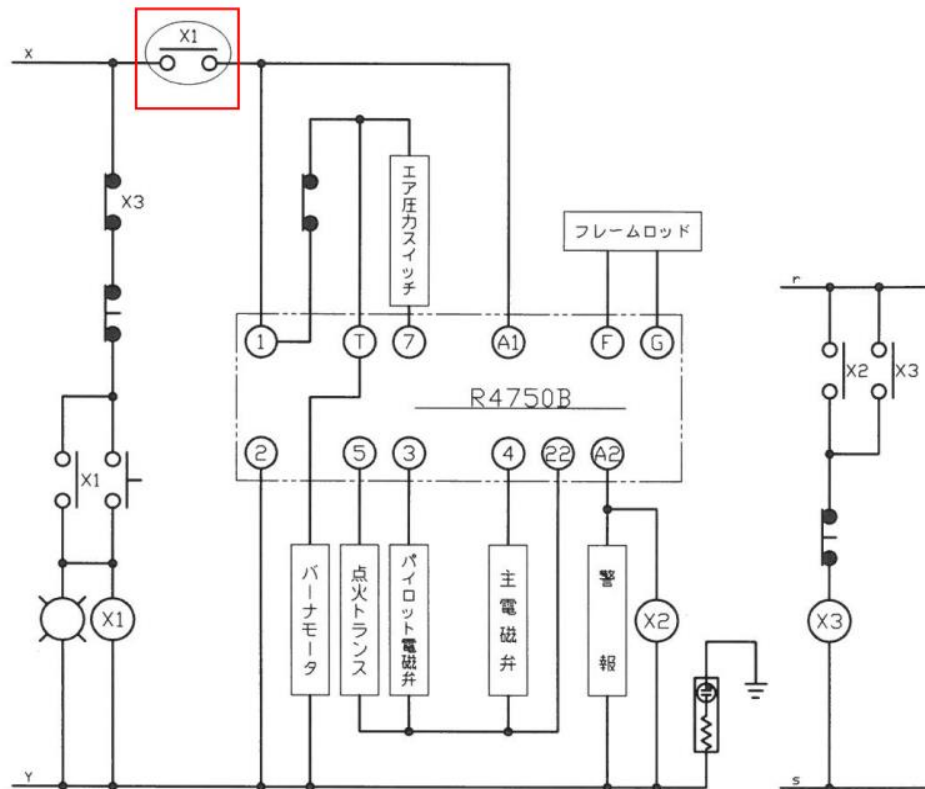
Case 1: Control circuit that Power to Burner control (Terminal 1) is Off when Alarm signal is generated.



Mesure : Change Start contact to between terminal 1 & terminal T.

R4750B to RCF502 (or RCF501)

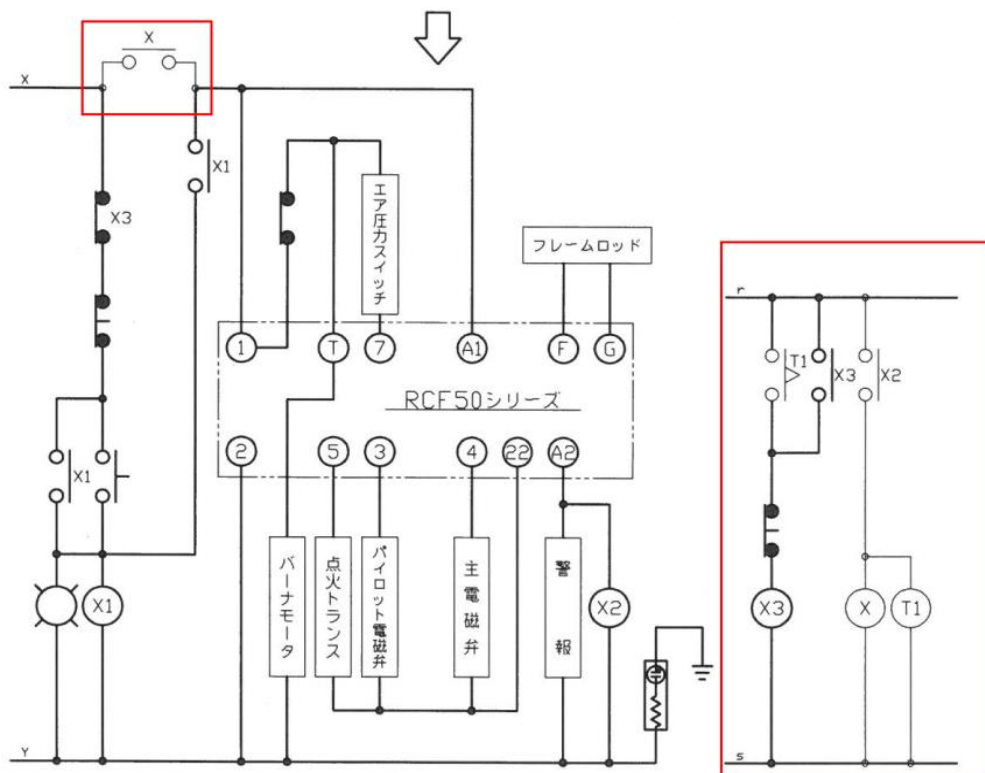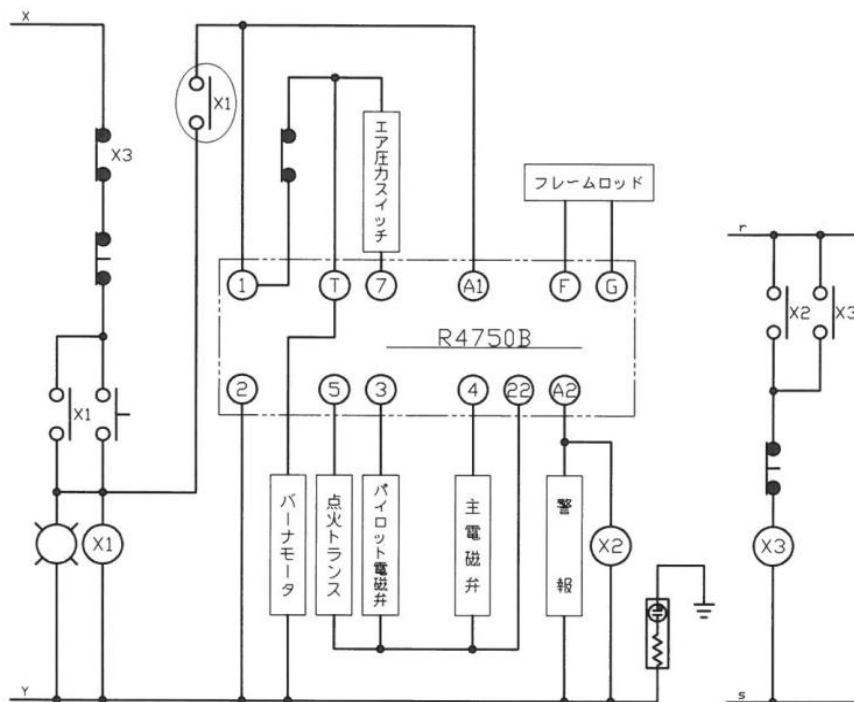
Case 1: Control circuit that Power to Burner control (Terminal 1) is Off when Alarm signal is generated.



Mesure : Add "Delay timer" as T1 and Relay as X. Power to Terminal 1 ON when Alarm is generated.

1901 0000 大英 2 月 10 日

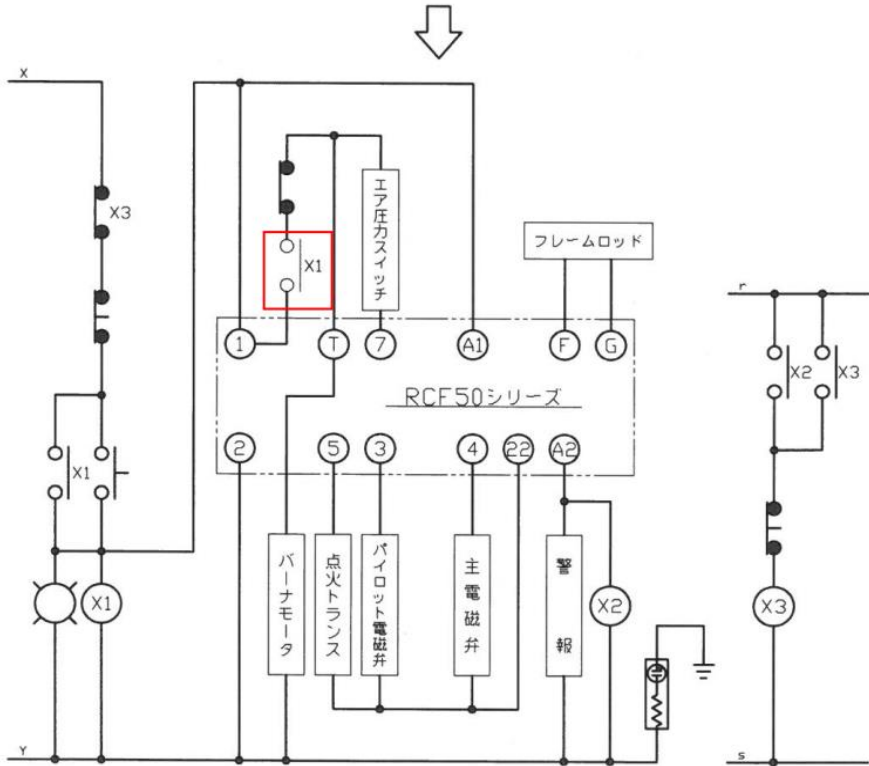Case 1: Control circuit that Power to Burner control (Terminal 1) is Off when Alarm signal is generated.



Mesure : Change Start contact to between terminal 1 & terminal T.